

Aman Kumar

Design and simulation of Two Stage OTA using LT Spice with a
DC Gain ≥ 60 dB, Unity Gain Freq ≥ 100 MHz for CL = 1 pF,
Phase Margin 50°-70°, Power dissipation <300 μ W





